

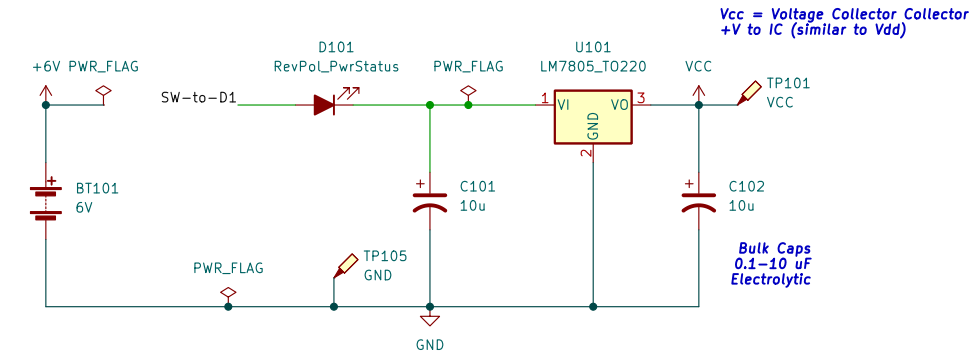
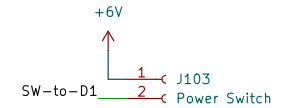





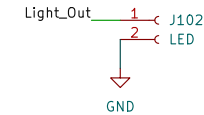
Submit a single PDF of the following:
 * Both sheets of the schematic
 * Screenshot showing 100% ERC validity
 * Screenshot of the Schematic Setup:Net Classes
 after you have assigned all net classes.



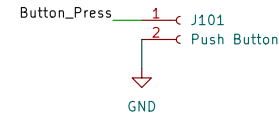The "Power" net class traces
 are a slightly different color.



Timers

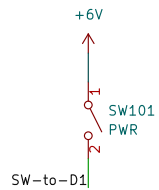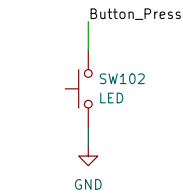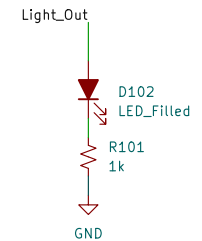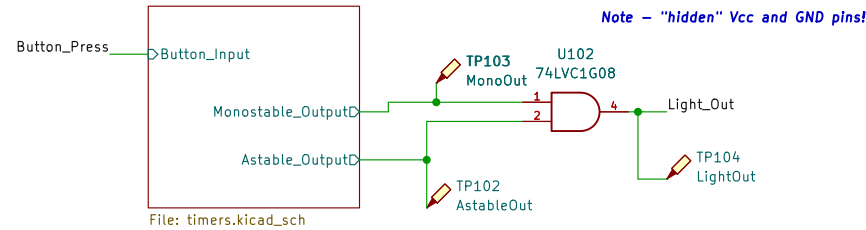

Note that all of the part annotations on this sheet are 1xx.

Duke | BME

Mark Palmeri

Sheet: /
 File: one-shot-blinking-light.kicad_sch


Title: One-Shot Blinking Light

Size: A4 Date: 2023-02-01
 KiCad E.D.A. kicad 6.0.10-2.fc37


Rev: v1.0.1
 Id: 1/2

Monostable One-Shot

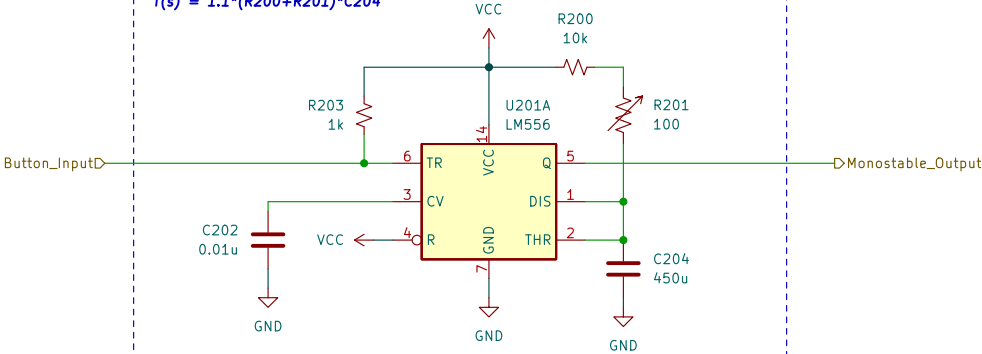$T(s) = 1.1 \cdot (R200 + R201) \cdot C204$



Astable Oscillator

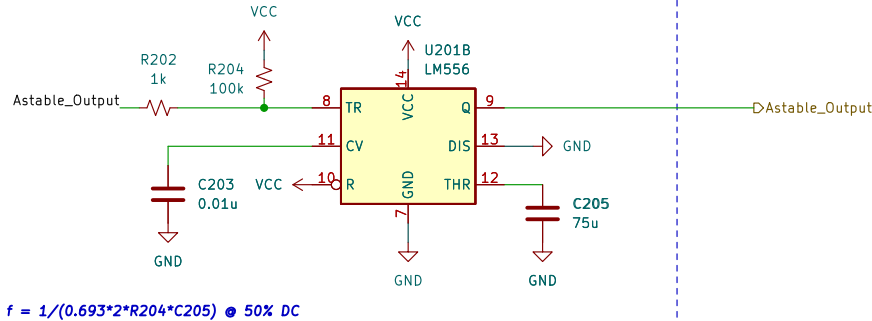

$f = 1 / (0.693 \cdot 2 \cdot R204 \cdot C205) @ 50\% DC$

Decoupling Cap
Power & Inductance
100 nF
Ceramic
(Physically place next to IC voltage pin.)

VCC
C201
100n
GND

Make sure your Page Settings data
is exported to all sheets.

Duke | BME

Mark Palmeri

Sheet: /Timers/
File: timers.kicad_sch

Title: One-Shot Blinking Light

Size: A4 Date: 2023-02-01
KiCad E.D.A. kicad 6.0.10-2.fc37

Rev: v1.0.1
Id: 2/2

Note that all of the part annotations on this sheet are 2xx.